

Learning Material - Experiment in ICT 2

Week 9


Goal of week

Student will be known about how to create a MUX, and use MUX to select data from 2 sources.

Content and requirement

Analyze Multiplexor, to design Multiplexor from OR, AND, NOT logic gate.

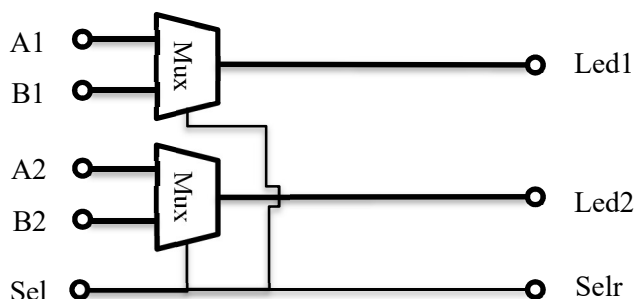Analyze the basic schematic below, and draw detail schematic circuit and assemble it in breadboard.



- A and B are two 2-bit sources. Student should connect A[1:2], B[1:2] to 4 buttons (*with pull-down resistor and led, view "Appliance User Guide"*)

- Sel is the selection signal. Student should plug Sel wire to the High voltage and Low voltage to make logic 0 and 1

- Led1, Led2, Selr wires are connected to Led to show values.

Experimental Equipment

- | | | | |
|------------------------|----|---------------------------------------|----|
| 1. Equipment Guideline | | 6. IC 74LS08 (AND) | x2 |
| 2. 5V Power | | 7. IC74LS04 (NOT) | x1 |
| 3. Breadboard | x1 | 8. Led | x8 |
| 4. Multimeter | x1 | 9. Resistor 330Ω | x8 |
| 5. IC 74LS32 (OR) | x1 | 10. Button A1, B1, A2, B2 (or switch) | x4 |

Experimental Steps

1. Analyze
2. Supply power and use multimeter test output state for each input conditions.

Experimental Report

All student must have a report, explain everything they does in this experiment with the content:

- Draw circuit's schematic.
- Inform all result getting from this experiment
- Give some remark