

Learning Material - Experiment in ICT 2

Week 13

Goal of week

Student will be known about sequential circuit, principles, structure and how to implement sequential circuit. Practice implement sequential circuit by design asynchronous BCD counter using D flip-flop

Content and requirement

Analyze principles, structure and activity of sequential circuit

Explore how to design a sequential circuit with specific function.

Implement asynchronous BCD counter using D flip-flop.

Experimental equipment



- | | | |
|---------------------|-----------------------|-----------------------|
| 1. IC 74LS74 (D-FF) | 5. IC 74LS86 (XOR) | 10. Voltmeter |
| 2. IC 74LS08 (AND) | 6. Function generator | 11. Conductors |
| 3. IC74LS00 (NAND) | 7. Resistors | 12. Oscilloscope |
| 4. IC 74LS32 (OR) | 8. Breadboard | 13. 7 segment display |
| | 9. 5VDC Power | |

Experimental Steps

1. Analyze principles and structure of asynchronous BCD counter using D flip-flop
 - Define input , output variable , state
 - Building truth table
 - Building excitation equations table
 - Assign state table
 - Define state diagram
 - Draw schematic circuit and assemble in breadboard
2. Analyze principles and structure of BCD counter using JK flip-flop
 - Define input , output variable , state
 - Building truth table and excitation equations table
 - Assign state table
 - Define state diagram
 - Draw schematic circuit and assemble in breadboard

Experimental Report

All students must have a report, explain everything you do in this experiment with the content:

- Draw circuit's schematic.
- Inform all result getting from this experiment
- Give some remark